

Charlieplexing Arduino - Controlling 12 LEDs with 4 GPIO Pins


Published August 6, 2019

1

A

Ashish Choudhary (/users/ashish-choudhary)

Author

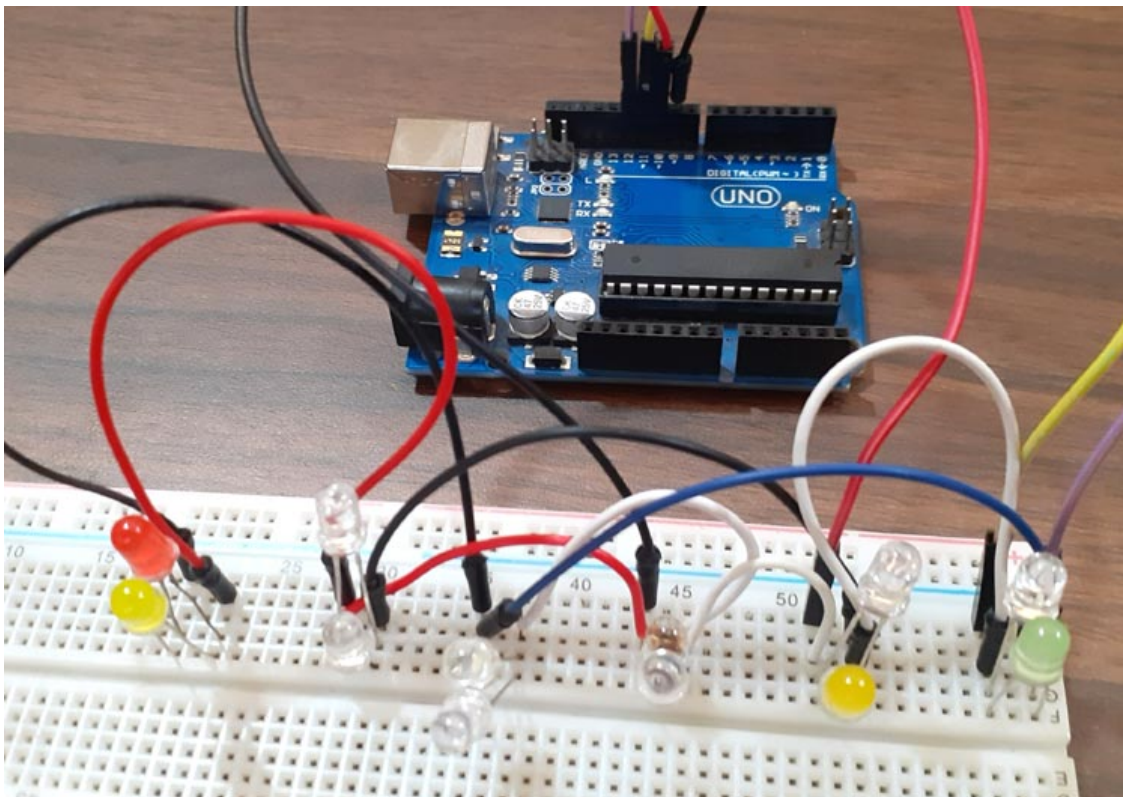

Charlieplexing Arduino- Controlling 12 LED with 4 GPIO Pins

Charlieplexing is a technique of controlling many LEDs using a few I/O pins. Charlieplexing is same as multiplexing, but it uses the tri-state logic (high, low input) to reduce the number of pins dramatically and to gain efficiency over multiplexing. The Charlieplexing technique is named after its inventor, Charlie Allen, who invented the technique in 1995. We previously used multiplexing technique in Arduino to [interface 4-digit 7-segment display](https://circuitdigest.com/microcontroller-projects/arduino-7-segment-display-clock) (<https://circuitdigest.com/microcontroller-projects/arduino-7-segment-display-clock>) and [driving 8x8 LED matrix](https://circuitdigest.com/microcontroller-projects/scrolling-text-display-on-8x8-led-matrix-arduino) (<https://circuitdigest.com/microcontroller-projects/scrolling-text-display-on-8x8-led-matrix-arduino>).


Charlieplexing allows you to control $N * (N - 1)$ LEDs, where N is the no of pins. For example, you can control 12 LEDs using 4 Arduino pins $4 * (4 - 1) = 12$. LEDs are diodes, and in diodes, current flows in only one direction. So in Charlieplexing, we connect two LEDs in parallel with each other but with opposite polarity so that only one LED turn on at a time. When it comes to Arduino or other microcontroller boards, you never have enough input/output pins. If you are working on a project in which you need to interface [LCD display \(https://circuitdigest.com/article/16x2-lcd-display-module-pinout-datasheet\)](https://circuitdigest.com/article/16x2-lcd-display-module-pinout-datasheet), a bunch of LEDs, and some sensors, then you are already out of pins. In that situation, you can charlieplex LEDs to reduce the number of pins.

In this tutorial, we are going to use **the Charlieplexing technique to control the 12 LEDs using 4 Arduino pins.**

Components Required

- Arduino UNO
- LED (12)
- 4 Resistor (330 ohms)
- Jumper Wires
- Breadboard

Circuit Diagram

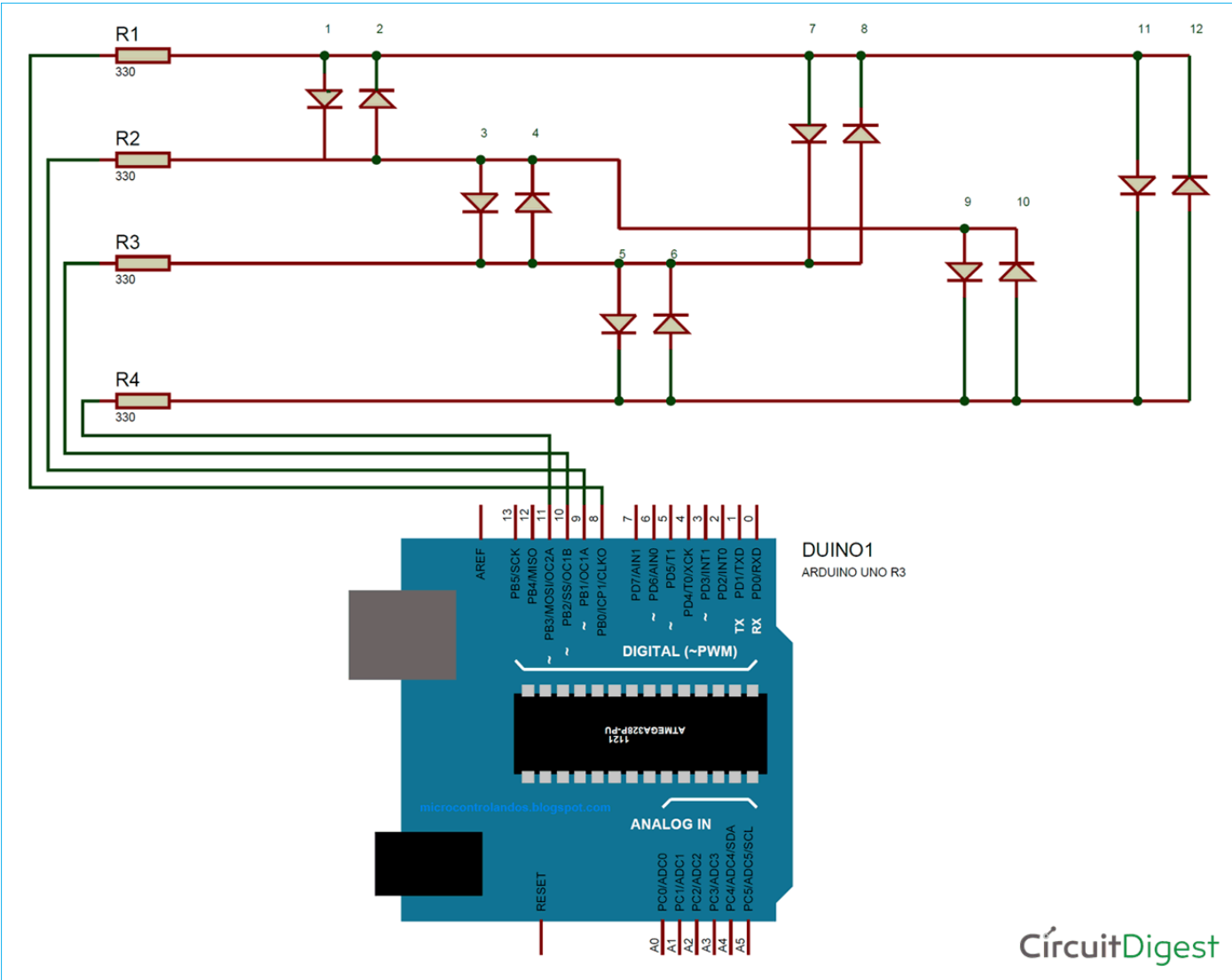


(./fullimage?i=circuitdiagram mic/Circuit-Diagram-for-Charlieplexing-Arduino-Controlling-12-LED-with-4-GPIO-Pins.png).

Basically, in this circuit diagram, 12 LEDs are connected with 4 Arduino pins through resistors. Each pin of Arduino is connected with three LEDs. There are six groups of LEDs, and in each group, 2 LEDs are connected, and both LEDs are parallel with each other but with opposite polarity so that only one LED turn on at a time. So according to the circuit diagram to turn on led 1, there needs to be a HIGH signal on pin A and a LOW signal on pin B, and pin C and D needs to be disconnected. The same procedure will be followed for the other LEDs. The full table of pin settings for each LED are given below:

LED	Pin 8	Pin 9	Pin 10	Pin 11
1	HIGH	LOW	INPUT	INPUT
2	LOW	HIGH	INPUT	INPUT
3	INPUT	HIGH	LOW	INPUT
4	INPUT	LOW	HIGH	INPUT
5	INPUT	INPUT	HIGH	LOW
6	INPUT	INPUT	LOW	HIGH

7	HIGH	INPUT	LOW	INPUT
8	LOW	INPUT	HIGH	INPUT
9	INPUT	HIGH	INPUT	LOW
10	INPUT	LOW	INPUT	HIGH
11	HIGH	INPUT	INPUT	LOW
12	LOW	INPUT	INPUT	HIGH

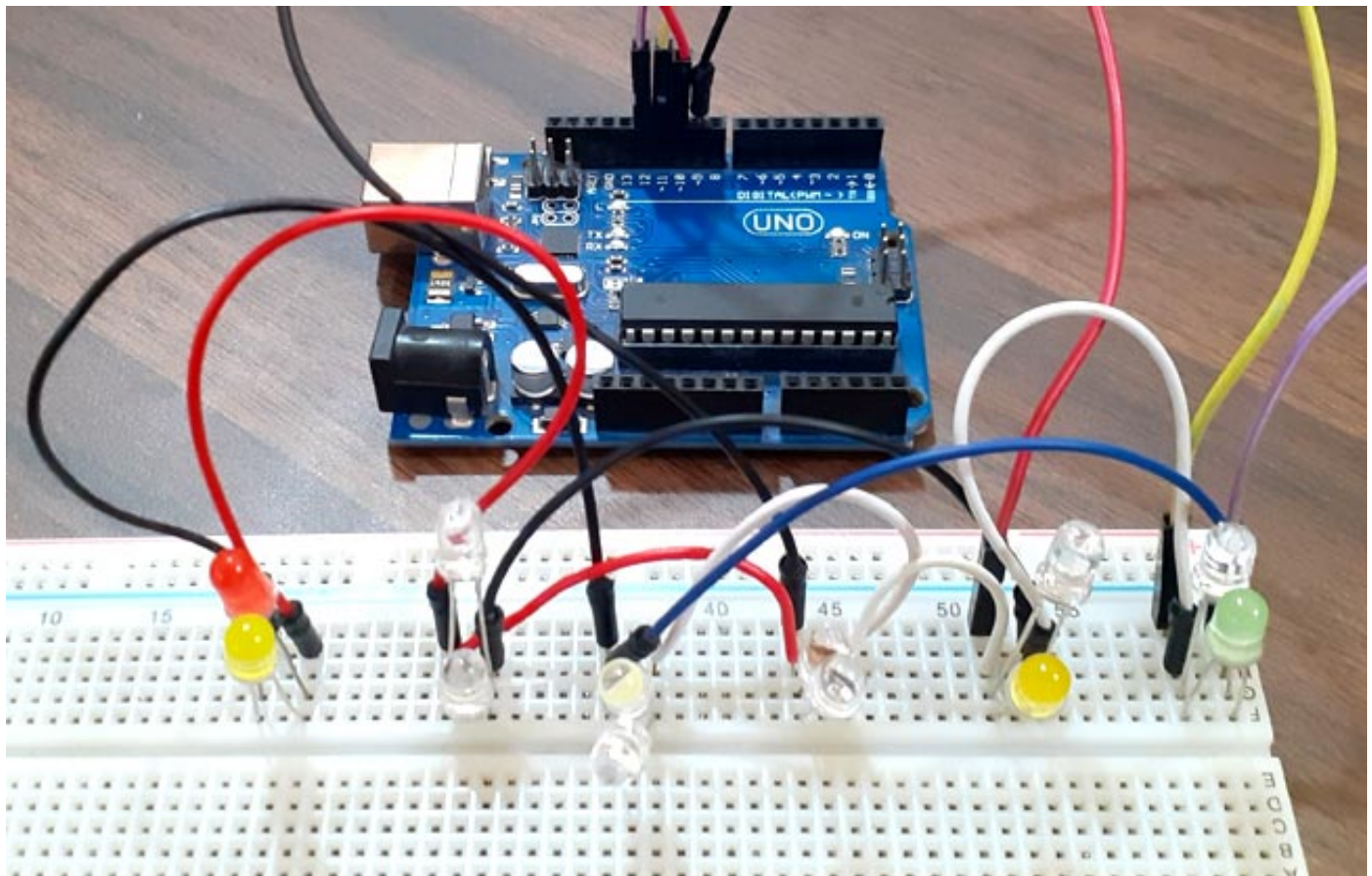After the connections my hardware looks like the image below. As you can see from image there are six groups of LEDs and in each group 2 LEDs are connected opposite to each other. The Arduino UNO module is powered by USB port.



Code Explanation

Complete code with a working video is given at the end of this tutorial, here we are explaining the complete program to understand the working of the project.

In the starting of Arduino code define all the pin at which LEDs are connected. After that, define the total number of LEDs and led state.

```
#define A 8
#define B 9
#define C 10
#define D 11
#define PIN_CONFIG 0
#define PIN_STATE 1
#define LED_Num 12
```


Now create a matrix for turning on and off LEDs in a sequence, you can change the sequence by changing the pin state and pin configuration. According to this matrix, LED1 will be turned on first then LED2 and so on.

```
int matrix[LED_No.][2][4] = {
  //          PIN_CONFIG          PIN_STATE
  //          A          B          C          D          A          B          C          D
  { { OUTPUT, OUTPUT, INPUT, INPUT }, { HIGH, LOW, LOW, LOW } },
  { { OUTPUT, OUTPUT, INPUT, INPUT }, { LOW, HIGH, LOW, LOW } },
  { { INPUT, OUTPUT, OUTPUT, INPUT }, { LOW, HIGH, LOW, LOW } },
  .....
  .....
}
```

Now inside the *void loop*, the program will execute the LED_COUNT matrix to turn on and off LEDs in the given sequence.

```
void loop() {
  for( int l = 0; l < LED_Num; l++ ) {
    lightOn( l );
    delay( 1000 / LED_Num );
  }
}
```

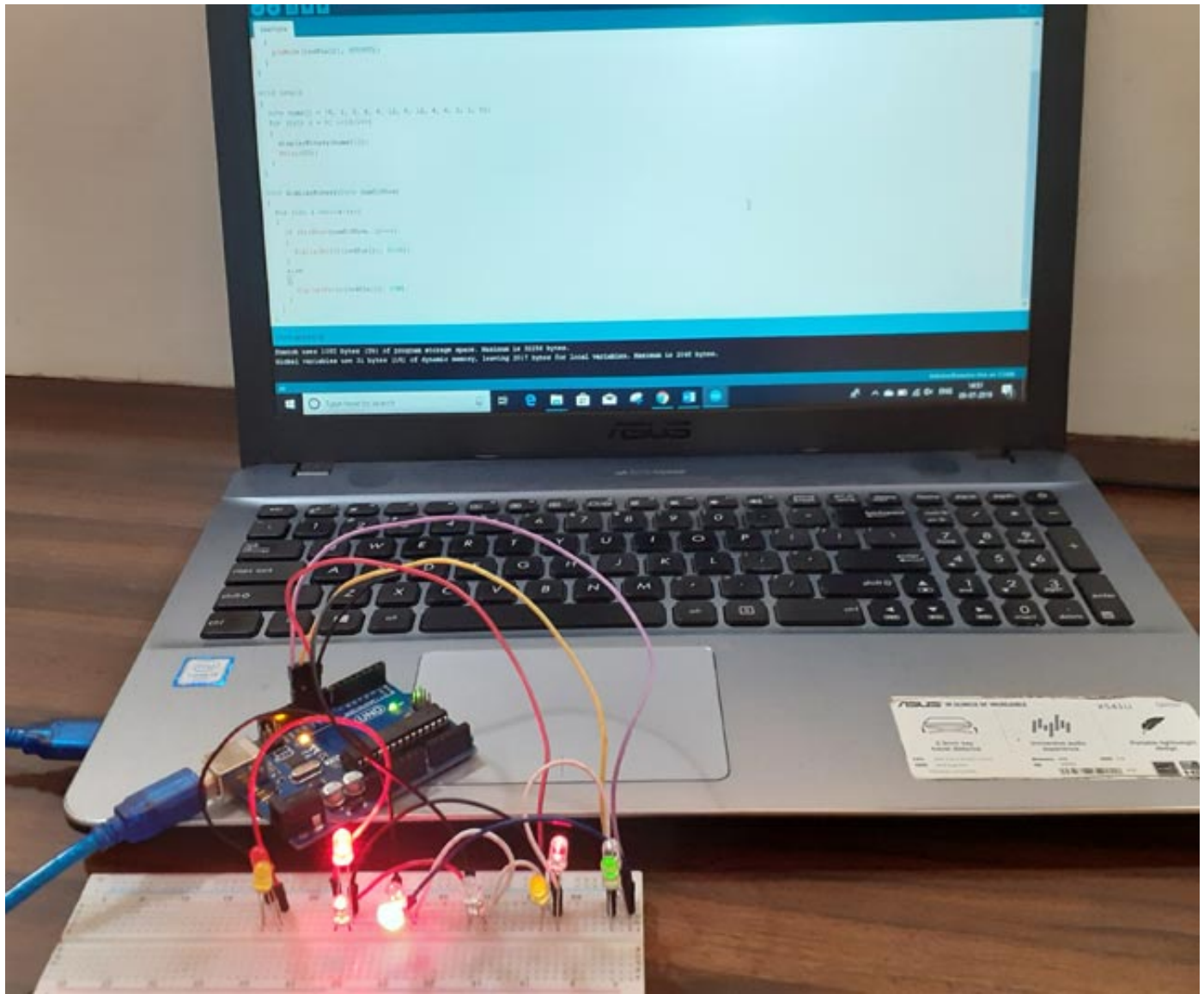Now connect the Arduino with the laptop and choose the board and port correctly and then click the Upload button. After uploading the code, your LEDs should start blinking.



So this is how **Charlieplexing technique** can be used to control many LEDs using fewer Arduino pins. You can use this method to control more number of LEDs. For example, if you want to control 20 LEDs, just edit the matrix and add the conditions for remaining LEDs.

Find the **complete code and working video** below.

Code

```

{ { OUTPUT, INPUT, OUTPUT, INPUT }, { LOW, LOW, HIGH, LOW } },
{ { OUTPUT, INPUT, INPUT, OUTPUT }, { HIGH, LOW, LOW, LOW } },
{ { OUTPUT, INPUT, INPUT, OUTPUT }, { LOW, LOW, LOW, HIGH } },
{ { INPUT, OUTPUT, INPUT, OUTPUT }, { LOW, HIGH, LOW, LOW } },
{ { INPUT, OUTPUT, INPUT, OUTPUT }, { LOW, LOW, LOW, HIGH } },
{ { INPUT, INPUT, OUTPUT, OUTPUT }, { LOW, LOW, HIGH, LOW } },
{ { INPUT, INPUT, OUTPUT, OUTPUT }, { LOW, LOW, LOW, HIGH } }
};

void lightOn( int led ) {
  pinMode( A, matrix[led][PIN_CONFIG][0] );
  pinMode( B, matrix[led][PIN_CONFIG][1] );
  pinMode( C, matrix[led][PIN_CONFIG][2] );
  pinMode( D, matrix[led][PIN_CONFIG][3] );
  digitalWrite( A, matrix[led][PIN_STATE][0] );
  digitalWrite( B, matrix[led][PIN_STATE][1] );
  digitalWrite( C, matrix[led][PIN_STATE][2] );
  digitalWrite( D, matrix[led][PIN_STATE][3] );
}

void setup() {}

void loop() {
  for( int l = 0; l < LED_Num; l++ ) {
    lightOn( l );
    delay( 1000 / LED_Num );
  }
}

```

Video

Charlieplexing Arduino - Controlling 12 LED with 4 GPIO Pins



Tags

[Arduino \(/Tags/Arduino\)](/Tags/Arduino)
[Arduino Uno \(/Tags/Arduino-Uno\)](/Tags/Arduino-Uno)
[Multiplexing \(/Tags/Multiplexing\)](/Tags/Multiplexing)
[LED \(/Tags/Led\)](/Tags/Led)

Comments

Submitted by Ron Barber (/users/ron-barber) on Sat, 01/16/2021 - 06:48

Permalink (/comment/33401#comment-33401)

Great nooby project, but be (/comment/33401#comment-33401)

Great nooby project, but be aware that the sketch is written to light the LEDs in a different order than 1-12.

As written, the sketch activates pins 8/9 (hi/low then low/high) , then 9/10, then 8/10, then 8/11, then 9/11 and finally 10/11. The diagram has the LEDs labelled in a different order.

Once you get the LEDs wired up correctly in a circle, it's pretty cool. Trying different delay values in the sketch makes it even more interesting!

Log in (/user/login?destination=/microcontroller-projects/charlieplexing-arduino-to-control-12-leds-with-4-gpio-pins%23comment-form) or register (/user/register?destination=/microcontroller-projects/charlieplexing-arduino-to-control-12-leds-with-4-gpio-pins%23comment-form) to post comments



G8PM DC Automotive PCB Relay (<https://bit.ly/3bdjm3u>)

Omron's G8PM DC Automotive PCB Relay is a high load automotive relay for motor/resistive control.

(<https://bit.ly/3bdjm3u>)



1552 Series ABS Plastic Enclosures (<https://bit.ly/3S8UieG>)

Hammond's 1552 series offers modern style and comfort with accessories that enhance capabilities.

(<https://bit.ly/3S8UieG>)



AVR-IoT Cellular Mini Development Board (<https://bit.ly/3KjeOW5>)

Microchip's AVR-IoT Cellular Mini features Sequans Monarch 2 GM02S cellular module

(<https://bit.ly/3KjeOW5>)



THA/THAS, Thinpack™, Aluminum Electrolytic Capacitors (<https://bit.ly/3zyRd06>)
Cornell Dubilier's THA/THAS Thinpack™ offers high energy density in a low-profile design

(<https://bit.ly/3zyRd06>)



K78 Series Non-Isolated DC/DC Switching Regulator (<https://bit.ly/3PWtv31>)
Mornsun's K78 series is a high-efficiency switching regulator with the packages of SiP, SMD, or DFN.

(<https://bit.ly/3PWtv31>)



Multi-Conductor Classics Cables (<https://bit.ly/3R7yePY>)
Belden's rugged multi-conductor cables ensure system uptime in rugged environments

(<https://bit.ly/3R7yePY>)



REVConnect RJ45 Connectors (<https://bit.ly/3bcklkj>)
Belden's REVConnect RJ45 Connectors fit Cat5e, Cat6, and Cat6A cables

(<https://bit.ly/3bcklkj>)



Traceability Solutions (<https://bit.ly/3To2bxo>)
Omron Automation Traceability Solutions
Omron's vast track, trace and control experience helps build...

(<https://bit.ly/3To2bxo>)



Join 100K+ Subscribers

Your email is safe with us, we don't spam.





Type your email address

Subscribe

Be a part of our ever growing community.



Semicon Media is a unique collection of online media, focused purely on the Electronics Community across the globe. With a perfectly blended team of Engineers and Journalists, we demystify electronics and its related technologies by providing high value content to our readers.

 (<https://www.facebook.com/circuitdigest/>)
  (<https://twitter.com/CircuitDigest>)
  (<https://www.youtube.com/channel/UCy3CUAIYgZdAOG9k3IPdLmw>)
  (<https://www.linkedin.com/company/circuit-digest/>)


COMPANY

[Privacy Policy \(/privacy-policy\)](/privacy-policy)
[Cookie Policy \(/cookie-policy\)](/cookie-policy)
[Terms of Use \(/terms-of-use\)](/terms-of-use)
[Contact](/contact)
[Us \(/contact\)](/contact)
[Advertise \(/advertise\)](/advertise)

PROJECT

[555 Timer Circuits \(/555-timer-circuits\)](/555-timer-circuits)
[Op-amp Circuits \(/op-amp-circuits\)](/op-amp-circuits)
[Audio Circuits \(/audio-circuits\)](/audio-circuits)
[Power Supply Circuits \(/smps-power-supply-circuits\)](/smps-power-supply-circuits)
[Arduino Projects \(/arduino-projects\)](/arduino-projects)
[Raspberry Pi Projects \(/simple-raspberry-pi-projects-for-beginners\)](/simple-raspberry-pi-projects-for-beginners)
[MSP430 Projects \(/msp430-projects\)](/msp430-projects)
[STM32 Projects \(/stm32-projects-and-tutorials\)](/stm32-projects-and-tutorials)
[ESP8266 Projects \(/esp8266-projects\)](/esp8266-projects)
[PIC Projects \(/pic-microcontroller-projects\)](/pic-microcontroller-projects)
[AVR Projects \(/avr-microcontroller-projects\)](/avr-microcontroller-projects)
[8051 Projects \(/8051-microcontroller-projects\)](/8051-projects)
[ESP32 Projects \(/esp32-projects\)](/esp32-projects)
[IoT Projects \(/internet-of-things-projects\)](/internet-of-things-projects)
[PCB Projects \(/diy-pcb-projects\)](/diy-pcb-projects)
[Arduino ESP8266 Projects \(/arduino-esp8266-projects\)](/arduino-esp8266-projects)
[All Microcontroller Projects \(/microcontroller-projects\)](/microcontroller-projects)

OUR NETWORK

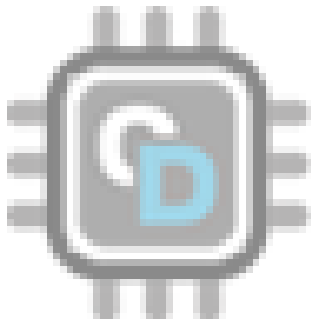


CIRCUIT DIGEST

(<https://circuitdigest.com>)

COMPONENTS¹⁰¹

(<https://components101.com>)

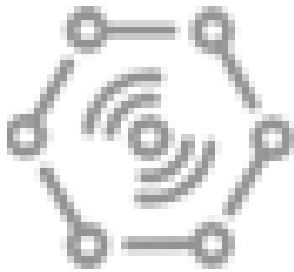

IOT DESIGN PRO

(<https://iotdesignpro.com>)

Copyright © 2022 Circuit Digest (/). All rights reserved.